# Electronic Musician

AN ACT III PUBLICATION
AUGUST 1990 VOL. 6, NO. 8

features
Why be normal? Mutate your signal processors into something new and different for \$20
Making the Groove  Keep your drum machine rockin' in rhythm with programming tips that'll make it sound like the real thing
Drum Machine Buyer's Guide
We'll help you compare and contrast the features and specs of myriad, marvelous machines before you buy that beat box
The Search for the Perfect Beat  Four veteran drum machine programmers discuss their techniques for creating hot, happenin' dance music
Signal Processing Today, Part 2: The Magic Of Real-Time MIDI Control  Take full advantage of your latest generation signal processor and add spice to your musical mix by making parameter changes "on the fly"



page 42

### reviews

#### First Takes and Quick Picks

DrumKAT MIDI Percussion Controller V. 2.0, Niche Audio Control Module (ACM), Valhala Sampling CDs, Kawai EQ-8 Parametric Equalizer, Anatek Uninterruptible Power Supply . . . . 84

Buchla Thunder
by Robert Rich
Vestax MR66
6-Track Cassette Recorder
by Gary Hall

## departments

The Front Page6
Letters
What's New
Service Clinic 82
Ad Index 98
Classifieds
FYI: For Your Information 113
The Back Page 114

**Cover:** Photograph by Mark Johann. Special thanks to Yamaha (RX8) and Alesis (HR-16:B).

Electronic Musician® is published at 6400 Hollis St. #12, Emeryville, CA 94608, and is ©1990 by NBB Acquisitions, Inc. This is Volume 6, Number 8, August 1990. Electronic Musician (ISSN: 0884-4720) is published monthly. Second Class postage paid at Oakland, CA, and additional mailing offices. All rights reserved. This publication may not be reproduced or quoted in whole or in part by any means, printed or electronic, without the written permission of the publishers.

page 30

Feedback can be your friend. Get more out of signal processors with this simple, clever, low-cost circuit.

BY DAVID SNOW

**ALTHOUGH I'M ALWAYS ON THE LOOKOUT** for gear with the best price/performance ratio, I'm usually compelled to sacrifice features for the sake of my budget. One of those sacrifices is knobs: Even though a device like the Alesis MIDIverb II has a large number of reverb, delay, flange, chorus, and stereo generation programs, I always want more. There isn't much you can do about modifying the MIDIverb's presets short of reprogramming its ROM (kids, don't try this at home), but as anyone who ever owned a spring reverb or a monophonic synth can tell you, there are innumerable ways to expand the application of any piece of equipment.

The May 1990 EM covered a MIDIverb-specific mod for adding *regeneration*, the technique of feeding a portion of the unit's output back into its input. But regeneration is just as applicable to plate reverbs, filters, vocoders, wa-wa pedals...you name it. Regeneration will turn a graphic equalizer into a nifty tone generator, and do things to spring reverbs that may be illegal in some states. The sonic results of regeneration depend upon the type of effect with which it is used: With simple delay, the input will echo, echo, echo and gradually fade away; with reverb, regeneration will introduce a metallic, artificial resonance. More commonly, adding regeneration to flangers produces an aggressive, swept-filter effect (and yes, using the exclusive secrets revealed herein you can psychedelicize the MIDIverb's ten flanging programs).

Best of all, this trick is easy to accomplish without modifying your equipment. All that's required is a mixer to combine the unit's output with its input, and a Y-connector to tap the output for monitoring (**Fig. 1**). While you could set up this configuration using mixer bus patching and a preamp or two, it's more convenient to build a small outboard mixer for this purpose and keep it hooked up to your unit. That's what the Retro-Regenerator project is all about.

#### RETRO-REGENERATOR

#### THE GRAND SCHEMATIC OF THINGS

The Retro-Regenerator (Fig. 2) is usable with virtually any stereo effects unit. Since both halves of the stereo circuit path are identical, we'll discuss just the left side to illustrate how it works.

Il couples the audio input into mixer ICla, which is followed by inverter IC1b; both are set to unity gain. IC1b restores the phase of the input signal, which ICla inverts. (Using the inverted signal will give a different sound in many instances. You might like to install a DPDT switch to select inverted or non-inverted feedback.—GH) IC1b's output then feeds into the signal processor's left input via J2. Output from the signal processor at J3 couples through regeneration-level pot R11a back into the mixer, while jack [4 parallels [3 to provide an output for the rest of your system. When switch S1 is in the bypass position, the feedback loop is out of the circuit.

The Retro-Regenerator requires a ripple-free, bipolar, 8 to 15V power supply; two 9-volt batteries will work, since current drain is low. I assembled my unit in an afternoon for less than \$10 using junkbox items and a few odds and ends from Radio Shack. Circuit construction isn't critical since we're not dealing with high-gain, high-frequency circuitry, but keep it neat, avoid bundling wires, re-

10k 10k left input to signal 2 10k processor left input regenerate bypass from signal R11a S1a processor R5 left output left R7 R9 output 10k 10k right input R8 J5 R6 to signal IC 1c processor right input regenerate bypass from signal R11b S<sub>1</sub>b 100k R10 right output 10k off O right output : DPDT battery power supply FIG. 2: Retro-Regenerator schematic.

main calm, stay to the right and pass to the left, and drink plenty of fluids. For that classically ugly art deco look, house it in an unpainted aluminum chassis decorated with labels from a Dymo label gun.

#### T'T'TALKIN' 'BOUT MY REGENERATION

A few guidelines will help you get the most from the Retro-Regenerator. First, unless you want to fry your tweeters and vaporize your eardrums, you should avoid runaway regeneration, which happens when the regenerated signal has a gain of more than one (in other words, each pass of the signal through the feedback loop increases in


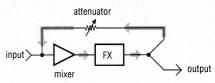


FIG. 1: Basic regeneration loop.

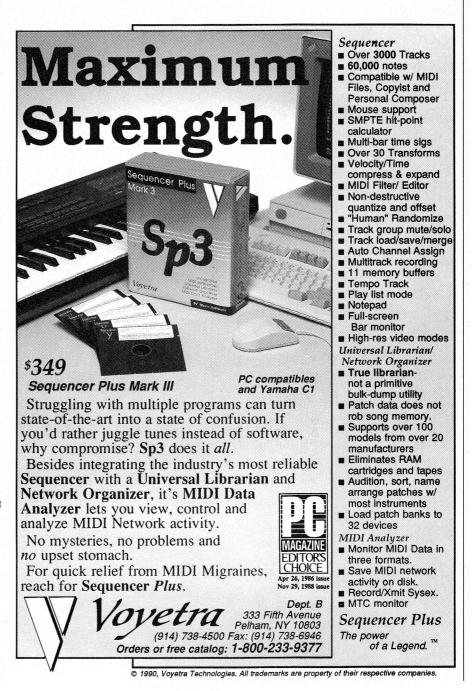level). It is possible to achieve musically useful effects using runaway feedback (as any recent David Myers tape will illustrate—CA), but all levels, at the Retro-Regenerator and the monitoring system, have to be carefully set. Second, in many cases (and particularly with the MIDIverb) the most pronounced regeneration effects occur with the signal



#### RETRO-REGENERATOR

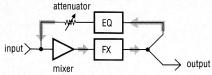


FIG. 3: Regeneration with equalization in loop.

processor output set as high as possible, although this increases the risk of going into uncontrolled feedback. So, to reconcile these competing considerations, here's a typical "calibration" procedure using the MIDIverb as an example:

1. Keep your power amp volume low.

- **2.** Set the MIDIverb Input pot to its minimum setting (7 o'clock position), set the Mix pot midway (12 o'clock position), and the Output pot to maximum (5 o'clock position).
- **3.** Set the Retro-Regenerator's regeneration pot to its maximum setting.
- **4.** With your input source at the maximum volume at which you intend to play, slowly open the MIDIverb input pot to the point just before the effect goes into feedback.
- **5.** Use the level pot on the Retro-Regenerator to introduce the amount of regeneration you want without worry-

#### **PARTS LIST** RESISTORS R1-R10 10k ( 1/4 watt, 5% carbon) R11 100k stereo control (Radio Shack #271-1732) SEMICONDUCTORS RC4136 or IC1 XR4136 quad op amp OTHER COMPONENTS 1/4-inch open cir-J1-J8 cuit phone jack S1 DPDT toggle switch Misc. Circuit board, enclosure, hookup wire,



# GOODMAN MUSIC

World's Largest Selection Of Keyboards, Synthesizers, Drum Machines, Samplers, Sequencers, MIDI, Pro Sound, & Multitrack Recording Gear!!!

> Every Major Brand Music Computers — Music Software CALL 1-800-842-4777

> > FAX 213-429-6543



LONG BEACH 4145 Viking Way (Near Intersectionsof Bellflower & Carson)

AA BREA/WILSHIRE 780 S La Brea Ave (3/4 bock South of Wilshire) (213) 937-2177 NORTH HOLLYWOOD 4227 N. Lankersheim Bvd. (1 Block N of Universal Studios) (818) 760-4430

WEST COVINA 544 Azusa Ave. (1 Block N. of the 10 Freeway) (818) 967-5767

SHERMAN OAKS 5631 Van Nuys Blvd. (2 Blocks N. of Ventura Blvd.) (818) 784-6900

MC, VISA, AE, OPTIMA, DISCOVER

ing about annoying squeals and howls.

knob, etc.

If you don't want to keep the MIDI-verb at its maximum ouput level, set it a couple of notches down and readjust the input level upwards for maximum effect, as just described. Some MIDI-verb programs are more prone to feedback than others and may require readjusting the input level as you switch from one to another. Also, variations in the input amplitude will affect the tendency to feed back as well.

Some Retro-Regenerator applications might not be obvious at first: Besides conventional flange, chorus, and delay enhancements, it works nicely with reverse reverb and bloom programs. It is also possible to insert signal processors (equalizers, delays, pitch shifters, etc.) into the feedback loop (Fig. 3) for more bizarre effects. So go ahead, be unpredictable! There are so many products being designed with cookie-cutter, corporate conceptions about music in mind that it's refreshing to throw a monkey-wrench into the works once in a while ... electronic music used to be experimental, after all. Here's your chance to create sounds you haven't heard before.

David Snow's interest in electronics was sparked by an issue of Popular Electronics he read ten years ago while a doctoral student in composition at Brandeis University. They kicked him out of the PhD program after a couple of years, but he seems to have turned out okay anyway.